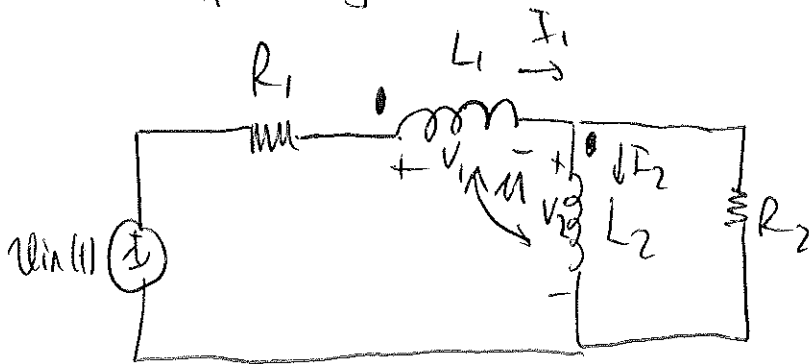


Q1

$v_{in}(t) = 10 \cos(t)$ Volt $\rightarrow \bar{V}_{in} = 10$
 $L_1 = 3$ Henry $L_2 = 3$ Henry $M = 1$ Henry

$(\omega = 1 \text{ rad/sec})$
 $R_1 = 1 \Omega$ $R_2 = 3 \Omega$

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} L_1 & M \\ M & L_2 \end{bmatrix} \begin{bmatrix} \frac{dI_1}{dt} \\ \frac{dI_2}{dt} \end{bmatrix}$$




In phasor domain

$\bar{V}_{in} = 10 \text{ V}$

$X_{R_1} = R_1$ $X_{R_2} = R_2$

$$\begin{bmatrix} \bar{V}_1 \\ \bar{V}_2 \end{bmatrix} = \begin{bmatrix} j\omega L_1 & j\omega M \\ j\omega M & j\omega L_2 \end{bmatrix} \begin{bmatrix} \bar{I}_1 \\ \bar{I}_2 \end{bmatrix}$$

circuit in phasor domain

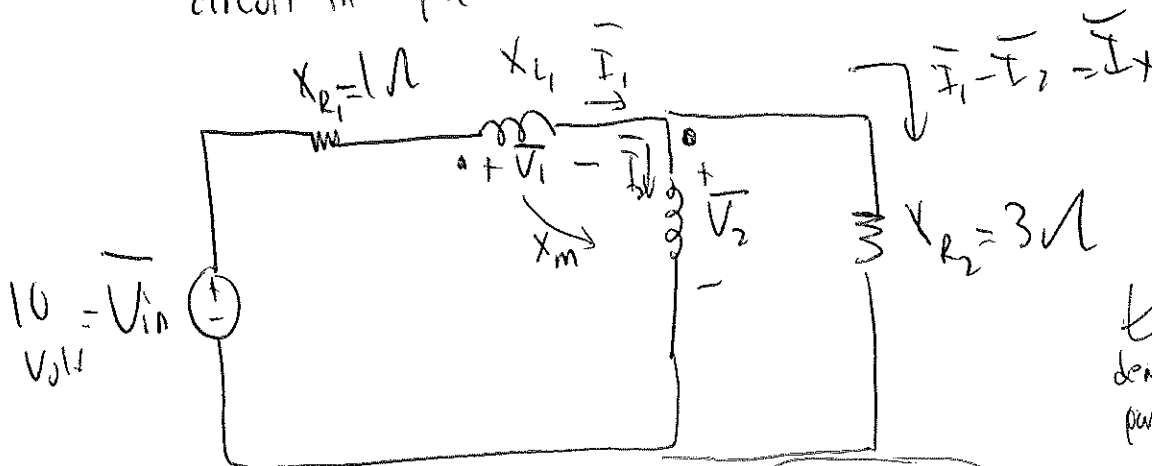

10 puan
 denklemleri parametreler denklemleri

$\bar{V}_{in} = \bar{I}_1 X_{R_1} + \bar{V}_1 + \bar{V}_2$ 5 puan

$10 = \bar{I}_1 \times 1 + [j\omega L_1 \bar{I}_1 + j\omega M \bar{I}_2] + [j\omega M \bar{I}_1 + j\omega L_2 \bar{I}_2]$

$10 = \bar{I}_1 + [3j \bar{I}_1 + j \bar{I}_2] + [j \bar{I}_1 + 3j \bar{I}_2]$

$10 = [1 + 4j] \bar{I}_1 + 4j \bar{I}_2$ 3 puan

$$\bar{V}_2 = X_{R_2} (\bar{I}_1 - \bar{I}_2) \quad (5 \text{ puan})$$

$$j\omega M \bar{I}_1 + j\omega L_2 \bar{I}_2 = 3 (\bar{I}_1 - \bar{I}_2)$$

$$(1-j) \bar{I}_1 + (3j+3) \bar{I}_2 = 0 \quad \bar{I}_1 = \frac{-(3j+3) \bar{I}_2}{1-j} = \frac{(3j+3) \bar{I}_2}{3-j} \quad (3 \text{ puan})$$

**

Put ** in *

$$10 = [1+4j] \frac{(3+3j) \bar{I}_2}{(3-j)} + 4j \bar{I}_2$$

$$10 = \frac{(3-12+15j)}{3-j} \bar{I}_2 + 4j \bar{I}_2$$

$$10(3-j) = [-9+15j] \bar{I}_2 + 4j(3-j) \bar{I}_2 \quad (3 \text{ puan})$$

$$30 - 10j = [-9+15j+12j+4] \bar{I}_2 \quad \frac{30-10j}{27j-4} = \bar{I}_2$$

$$\bar{I}_1 = \frac{3(j+1)}{3-j} \bar{I}_2 = \frac{3(j+1)}{3-j} \frac{30-10j}{27j-4} = \frac{3(j+1) \times 10(3-j)}{3-j(27j-4)} \quad (3 \text{ puan})$$

$$\bar{I}_x = \bar{I}_1 - \bar{I}_2 = \frac{30j+36}{27j-4} - \left[\frac{30-10j}{27j-4} \right]$$

$$\bar{I}_x = \frac{40j}{27j-4} = \frac{40j^2}{27j^2-4j} = \frac{-40}{-27-4j} = \frac{40}{27+4j} = 40 \frac{27-4j}{27^2+4^2} \text{ A}$$

(3 puan)


$$P_{R_2} = \frac{1}{2} R_2 \bar{I}_x \bar{I}_x^* = \frac{1}{2} \times 3 \times \left[40 \frac{27-4j}{27^2+4^2} \right] \left[40 \frac{27+4j}{27^2+4^2} \right]$$

$$= \frac{1}{2} \times 3 \times \frac{40^2}{27^2+4^2} = \frac{1}{2} \times 3 \times \frac{40^2}{27^2+4^2} = \frac{2400}{27^2+4^2} \text{ Watt}$$

Q2) $h(t) = u(t)$ $u_{in}(t) = e^{-t}$


$$u_{out}(t) = \int_{-\infty}^t h(t-\tau) u_{in}(\tau) d\tau$$

$t < 0$

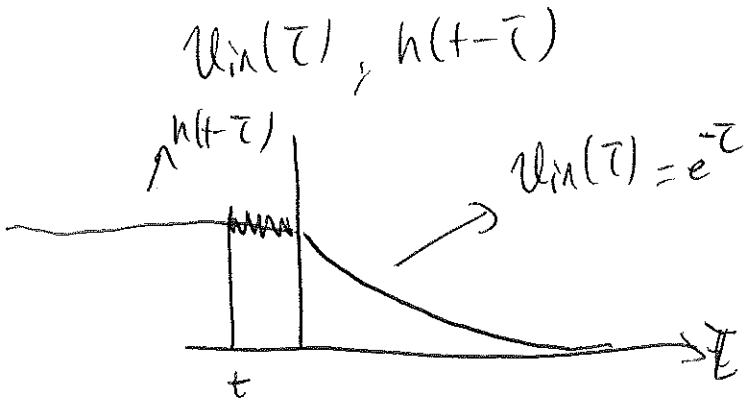

5 puan
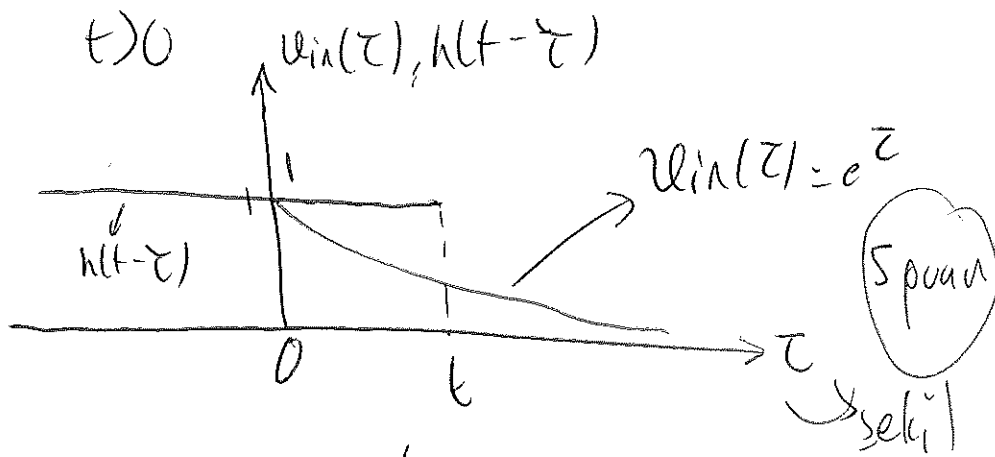
$$u_{out}(t) = \int_{-\infty}^t h(t-\tau) u_{in}(\tau) d\tau = 0$$



result

$$u_{out}(t) = \begin{cases} 0, & t < 0 \\ 1 - e^{-t}, & t > 0 \end{cases}$$

$$u_{out}(t) = \int_{-\infty}^t h(t-\tau) u_{in}(\tau) d\tau$$

$$= \int_{-\infty}^0 h(t-\tau) u_{in}(\tau) d\tau + \int_0^t h(t-\tau) u_{in}(\tau) d\tau$$

$$= \int_{-\infty}^0 1 \times 0 d\tau + \int_0^t 1 \cdot e^{-\tau} d\tau$$

$$u_{out}(t) = 0 - e^{-\tau} \Big|_0^t = -[e^{-t} - e^0] = 1 - e^{-t}$$


10 puan

(Q3)

$X_{e1} = 12 \Omega$

$P_{source} = 400 \text{ Watt}$

$Q_{source} = -300 \text{ VAR}$

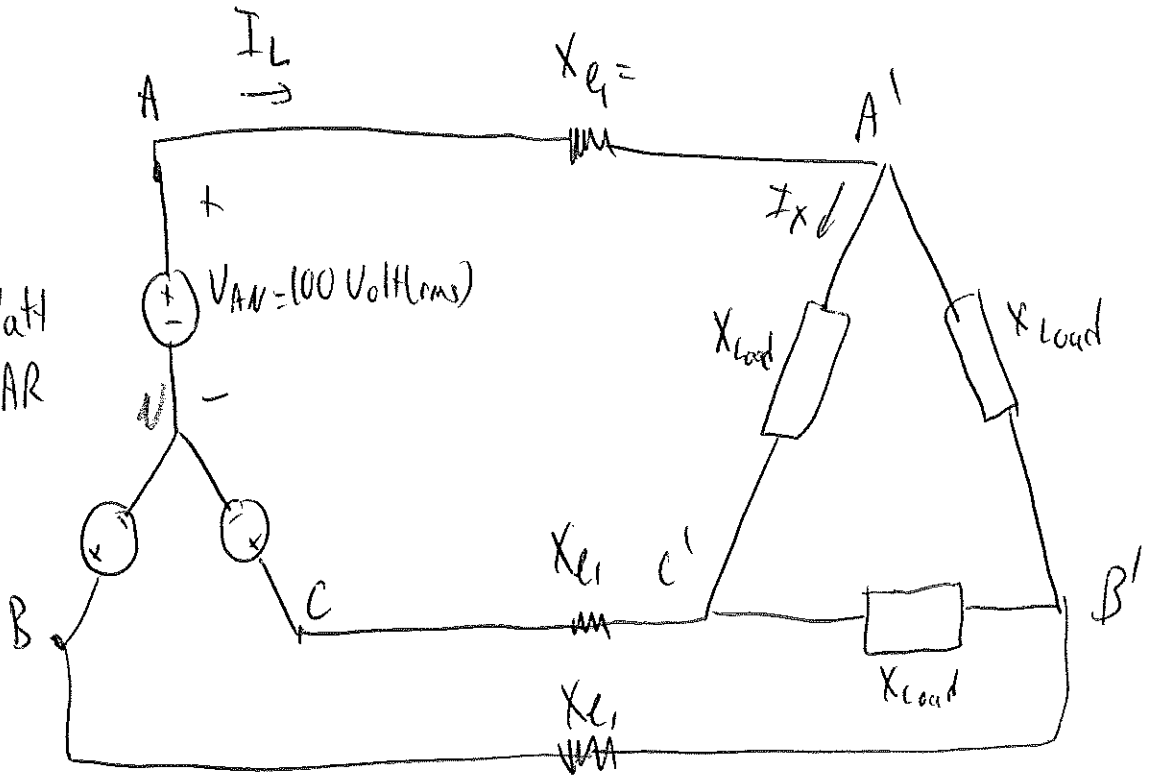

$S_{source} = \sqrt{(P_{source})^2 + (Q_{source})^2}$

$|S_{source}| = \sqrt{(400)^2 + (-300)^2} = 500 \text{ VA}$ (2 pua)

$3 |V_{AN}| |I_{L1}| = |S_{source}|$

$|I_{L1}| = \frac{500}{3 \times 100} = \frac{5}{3} \text{ Ampere}$ (2 pua)

$|V_{A'C'}| = 100 \sqrt{3} \text{ Volt (rms)}$ (2 pua)

$P_{line} = 3 |I_{L1}|^2 \text{Re}\{X_{e1}\}$ (2 pua)
 $= 3 \left(\frac{5}{3}\right)^2 \cdot 12 = 100 \text{ Watt}$

$Q_{line} = 3 |I_{L1}|^2 \text{Im}\{X_{e1}\}$ (2 pua)
 $= 0 \text{ VAR}$

$P_{Load} = P_{source} - P_{line} = 400 - 300 = 300 \text{ Watt}$ (2 pua)


$Q_{Load} = Q_{source} - Q_{line} = -300 - 0 = -300 \text{ VAR}$ (2 pua)

$|S_{Load}| = \sqrt{P_{Load}^2 + Q_{Load}^2} = 300 \sqrt{2} \text{ VA}$ (2 pua)

$|V_{A'C'}| = \frac{|S_{Load}|}{\sqrt{3} |I_{L1}|} = \frac{300 \sqrt{2}}{\sqrt{3} \cdot \frac{5}{3}} = 60 \sqrt{6} \text{ Volt}$ (2 pua)

$|I_{x1}| = \frac{|I_{L1}|}{\sqrt{3}} = \frac{5}{3\sqrt{3}} \text{ Ampere (rms)}$ (2 pua)

Q.4.

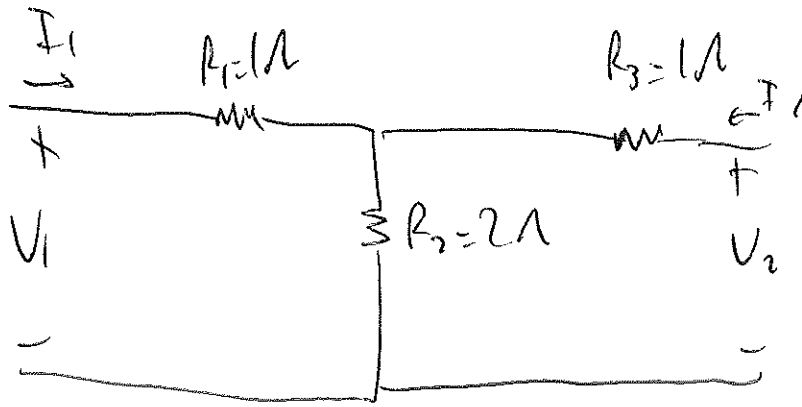

$$V_1 = R_1 I_1 + R_2 (I_1 + I_2) \quad V_2 = R_3 I_2 + R_2 (I_1 + I_2)$$

$$V_1 = (R_1 + R_2) I_1 + R_2 I_2 \quad V_2 = R_2 I_1 + (R_2 + R_3) I_2$$

$$V_1 = 3 I_1 + 2 I_2 \quad V_2 = 2 I_1 + 3 I_2$$

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 3 & 2 \\ 2 & 3 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$