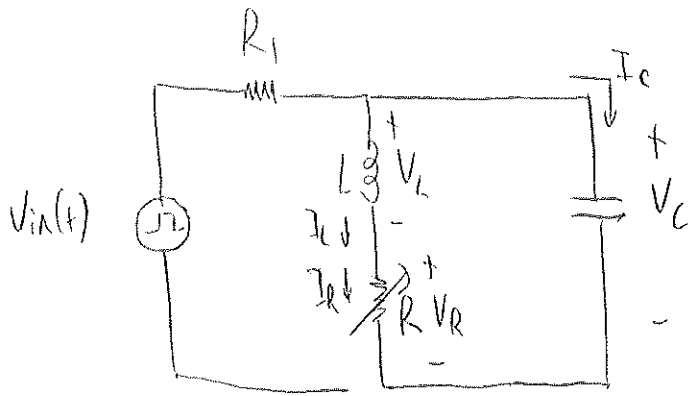


LAB-2 (ECE 232) (continue)

(1)



$$R_1 = 10k\Omega$$

$$R = 10k\Omega \text{ pot}$$

$$L = 0.1 \text{ Henry}$$

$$C = 0.1 \mu\text{F}$$

Differential equations.

$$\frac{d^2 V_c}{dt^2} + \left(\frac{1}{R_1 C} + \frac{R}{L} \right) \frac{dV_c}{dt} + \left(\frac{R}{R_1 L C} + \frac{1}{L C} \right) V_c = \frac{R}{R_1 L C} V_{in}(t)$$

characteristic equation $s^2 + \left(\frac{1}{R_1 C} + \frac{R}{L} \right) s + \left(\frac{R}{R_1 L C} + \frac{1}{L C} \right) = 0$

$$2\alpha = \left(\frac{1}{R_1 C} + \frac{R}{L} \right)$$

$$\omega_0^2 = \left(\frac{R}{R_1 L C} + \frac{1}{L C} \right)$$

$$2\alpha = 1000 + 10R$$

$$\omega_0^2 = 10^4 R + 10^8$$

$$\alpha = 500 + 5R$$

$$\omega_0 = 10^2 \sqrt{R + 10^4}$$

When DC input is applied [assume $V_{in}(t) = 1 \text{ Volt}$]

$V_c(t) = V_{cp} + V_{ch}$ put V_{cp} in diff equation [$V_{cp} = K$ constant]

$$\frac{d^2}{dt^2} K + \left(\frac{1}{R_1 C} + \frac{R}{L} \right) \frac{dK}{dt} + \left(\frac{R}{R_1 L C} + \frac{1}{L C} \right) K = \frac{R}{R_1 L C} \cdot 1 \rightarrow K = \frac{\frac{R}{R_1 L C}}{\frac{R}{R_1 L C} + \frac{1}{L C}}$$

$$K = \frac{R 10^4}{R 10^4 + 10^8} = V_{cp} \quad \left(\begin{array}{l} \text{For underdamped} \\ \text{overdamped and} \\ \text{critically-damped} \\ \text{cases} \end{array} \right)$$

(2)

$$\frac{d^2 I_c}{dt^2} + \left(\frac{R}{L} + \frac{1}{R_0 C} \right) \frac{dI_c}{dt} + \left(\frac{1}{LC} + \frac{R}{LR_0 C} \right) I_c = \frac{V_{in}}{LR_0 C}$$

assume DC input is applied ($V_{in} = 1 \text{ Volt}$) $I_{cp} = \text{??}$

put I_{cp} in diff equation

$$\frac{d^2 M}{dt^2} + \left(\frac{R}{L} + \frac{1}{R_0 C} \right) \frac{dM}{dt} + \left(\frac{1}{LC} + \frac{R}{LR_0 C} \right) M = \frac{1}{LR_0 C}$$

$$M = \frac{\frac{1}{LR_0 C}}{\frac{1}{LC} + \frac{R}{LR_0 C}} = \frac{10^4}{R \cdot 10^4 + 10^8} \quad \left(\begin{array}{l} \text{For underdamped} \\ \text{overdamped and} \\ \text{critically damped} \\ \text{cases} \end{array} \right)$$

$$V_c(t) = V_{cp} + V_{ch}$$

$$I_c(t) = I_{cp} + I_{ch}$$

roots of characteristic equation $s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$

$$s_{1,2} = -(500 + 5R) \pm \sqrt{(500 + 5R)^2 - (10^4 R + 10^8)}$$

For critically-damped case $\alpha = \omega_0$ $(500 + 5R_0) = 10^2 \sqrt{R_0 + 10^4}$

$$R_0^2 - 400R_0 - 3990000 = 0 \rightarrow \text{roots } R_{0,1,2} = \frac{+400 \pm 4014.97}{2}$$

$$R_{0,1} \approx 2207$$

$$R_{0,2} = -1807.48$$

(not possible)

Hence when $R = R_0 = 2207 \Omega$ (system is critically damped) //

(*)

when

(3)

$$0 < R < R_0 \quad 0 < R < 2207 \quad (\text{the system is underdamped})$$

$$s_{1,2} = -(500 + 5R) \pm j \sqrt{(10^6 R + 10^8) - (500 + 5R)^2}$$

$$\text{assume } R = \frac{R_0}{4} = 551.75 \quad \rightarrow V_{cp} = 0.0522 \text{ Volt}$$

$$I_{cp} = 9.4778 \times 10^{-5} \text{ Amper}$$

$$s_{1,2} = -3255 \mp j 9742.4$$

$$V_c(t) = V_{cp} + V_{ch} = 0.0522 + e^{-3255t} \left[A_1 \cos(9742.4t) + A_2 \sin(9742.4t) \right]$$

$$I_L(t) = I_{cp} + I_{ch} = 9.4778 \times 10^{-5} + e^{-3255t} \left[B_1 \cos(9742.4t) + B_2 \sin(9742.4t) \right]$$

$$\lim_{t \rightarrow \infty} V_c(t) = 0.0522 \text{ Volt} //$$

$$V_R(t) = R I_L(t)$$

$$\lim_{t \rightarrow \infty} I_L(t) = 9.4778 \times 10^{-5} \text{ Amper} //$$

$$V_L(t) = L \frac{dI_L}{dt}$$

$$\lim_{t \rightarrow \infty} V_R(t) = \lim_{t \rightarrow \infty} V_c(t) = 0.0522 \text{ Volt} //$$

$$\lim_{t \rightarrow \infty} V_L(t) = 0 \text{ Volt} //$$

**

when

$$R > R_0 \quad R > R_0 = 2207 \Omega$$

$$s_{1,2} \approx -11535 \quad \rightarrow V_{cp} = 0.1808 \text{ Volt}$$

$$\rightarrow I_{cp} = 8.1920 \times 10^{-5} \text{ Amper}$$

$$V_c(t) = V_{cp} + V_{ch} = 0.1808 + e^{-11535t} (A_1 t + A_2) \quad (\text{Volt})$$

$$I_L(t) = I_{cp} + I_{ch} = 8.1920 \times 10^{-5} + e^{-11535t} (B_1 t + B_2) \quad (\text{Amper})$$

$$V_R = R I_L(t)$$

$$V_L = L \frac{dI_L}{dt}(t)$$

$$\lim_{t \rightarrow \infty} V_c(t) = 0.1808$$

$$\lim_{t \rightarrow \infty} I_L(t) = 8.1920 \times 10^{-5} \text{ Amper}$$

$$\lim_{t \rightarrow \infty} V_L(t) = 0 \text{ Volt}$$

$$\lim_{t \rightarrow \infty} V_R(t) = \lim_{t \rightarrow \infty} V_c(t) = 0.1808 \text{ Volt}$$

(9)

$$R = 3R_0 = 6621 \Omega$$

$$s_1 = -2571.4 //$$

$$V_{cp} = 0.3984 \text{ Volt}$$

$$s_2 = -64639 //$$

$$I_{cp} = 6.0165 \times 10^{-5} \text{ Amper}$$

$$V_L(t) = 0.3984 + A_1 e^{-2571.4t} + A_2 e^{-64639t}$$

$$I_L(t) = 6.0165 \times 10^{-5} + B_1 e^{-2571.4t} + B_2 e^{-64639t}$$

$$\lim_{t \rightarrow \infty} V_L(t) = 0.3984 \text{ Volt}$$

$$\lim_{t \rightarrow \infty} I_L(t) = 6.0165 \times 10^{-5} \text{ Amper}$$

$$\lim_{t \rightarrow \infty} V_R(t) = \lim_{t \rightarrow \infty} R I_L(t) = 0.3984 \text{ Volt}$$

$$\lim_{t \rightarrow \infty} V_C(t) = 0 \text{ Volt}$$

Assume input is $V_{in}(t) \rightarrow$ square wave with $f = 150 \text{ Hz}$

$$\text{if } f = 150 \text{ Hz} \quad T = \frac{1}{150} = 6.7 \text{ ms}$$

compare T with τ values for each case

$$\begin{aligned} * \text{ Overdamped } \quad R > 3R_0 \quad s_1 = -2571.4 \quad s_2 = -64639 \quad \tau_1 = \frac{1}{|s_1|} \quad \tau_2 = \frac{1}{|s_2|} \\ \tau_1 = 0.3889 \text{ ms} \quad \tau_2 = 0.015471 \text{ ms} \end{aligned}$$

$T \gg \tau_{1,2}$ [square wave can be thought as a DC input since $T \gg \tau_{1,2}$]

Hence $V_L(t)$ and $I_L(t)$ [in general the circuit] will go into steady-state condition

(5)

* Critically damped $s_{1,2} = -11535$

$R = R_0$ $T_1 = 0.08192 \text{ ms}$ $T_2 = 0.08192 \text{ ms}$

$T = 6.7 \text{ ms} \gg T_{1,2}$ [square wave can be thought as a DC input since $T \gg T_{1,2}$]

Hence $V_c(t)$ and $I_c(t)$ will quickly reach to steady-state condition.

* Underdamped case $s_{1,2} = -3255 \pm j 9742.4$

$R = \frac{1}{4} R_0 = 551.75$ $T_{1,2} = 0.30777 \text{ ms}$ $T = 0.67 \text{ ms} \gg T_{1,2}$

$T_{1,2} = \frac{1}{|\text{Real}(s_{1,2})|}$ square wave can be thought as a DC input

$V_c(t)$ and $I_c(t)$ will reach steady-state very quickly.

