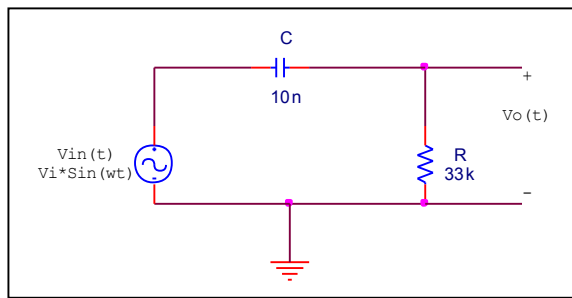


ECE 232-Lab5

Low-pass and High-pass filters

1. Consider the high pass filter below its frequency response is $H(j\omega)=V_o(j\omega)/V_{in}(j\omega)$



Fill in the table below due to your observations on the oscilloscope and sketch the magnitude and phase response (only due to the observations in YT mode) using MATLAB.


High-pass filter	YT-mode	YT-mode	XY-mode	XY-mode
f(Hz)	$ H(j\omega) $	$\angle H(j\omega)$	$ H(j\omega) $	$\angle H(j\omega)$
$f \approx 20$				
$f = 200$				
$f = f_c$ (half power frequency)				
$f = 1000$				
$f = 5000$				

What is the half-power frequency f_c ?

What is the half-power angular-frequency ω_c ?

2- When the switch S is open the circuit below becomes a low-pass filter and its frequency response is

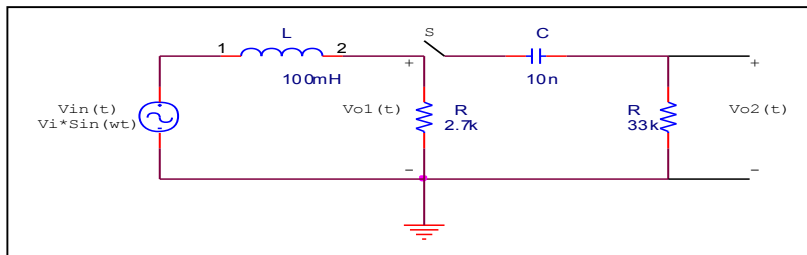$H(j\omega)=V_{o1}(j\omega)/V_{in}(j\omega)$. Fill in the table below due to your observations on the oscilloscope and sketch the magnitude and phase response (only due to the observations in YT mode) using MATLAB.



Fill in the table below due to your observations on the oscilloscope and sketch the magnitude and phase response (only due to the observations in YT mode) using MATLAB.

Low-pass filter	YT-mode	YT-mode	XY-mode	XY-mode
f(Hz)	$ H(j\omega) $	$\angle H(j\omega)$	$ H(j\omega) $	$\angle H(j\omega)$
$f \approx 20$				
$f = 2000$				
$f = f_c$ (half power frequency)				
$f = 6000$				

What is the half-power frequency f_c ?

What is the half-power angular-frequency ω_c ?