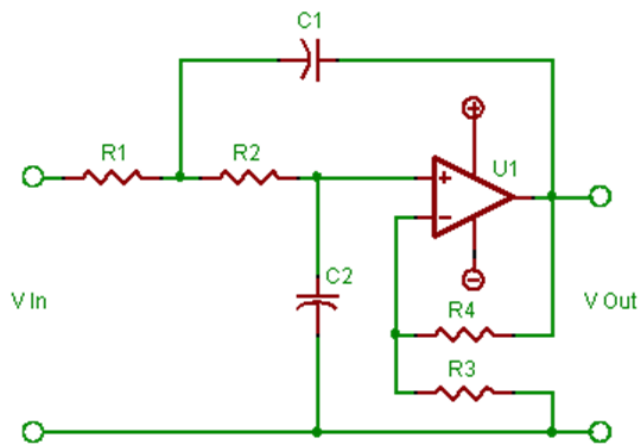


## ECE 232 – Advanced Electrical Circuit Analysis

## Lab6

## Preliminary Work:

## 1. Second order low-pass filter



$$c_1 = c_2 = 0.1\mu\text{F}$$

$$R_1 = R_2 = 1.2\text{k}\Omega$$

$$R_3 = R_4 = 1\text{k}\Omega$$

$$V_- = V_o \frac{R_3}{R_3 + R_4} = \frac{V_o}{2} = V_+ \quad \text{in linear mode}$$

1<sup>st</sup> node equation for  $V_+ = \frac{V_o}{2}$  ;

$$\frac{V_o/2}{1/sC_2} + \frac{V_o/2 - V_x}{R_2} = 0$$

$$V_x = V_o \left( \frac{sR_2C_2}{2} + \frac{1}{2} \right) \quad (\text{eqn} - 1)$$

2<sup>nd</sup> node equation for  $V_x$  ;

$$\frac{V_x - V_o/2}{R_2} + \frac{V_x - V_o}{1/sC_1} + \frac{V_x - V_i}{R_1} = 0$$

$$\frac{V_i}{R_1} = V_x \left( \frac{1}{R_1} + sC_1 + \frac{1}{R_2} \right) - V_o \left( sC_1 + \frac{1}{2R_2} \right)$$

From eqn-1

$$\frac{V_i}{R_1} = V_o \left( \frac{sR_2C_2}{2} + \frac{1}{2} \right) \left( \frac{1}{R_1} + sC_1 + \frac{1}{R_2} \right) - V_o \left( sC_1 + \frac{1}{2R_2} \right)$$

$$\frac{V_i}{R_1} = V_o \left( \frac{sR_2C_2}{2R_1} + \frac{1}{2R_1} + \frac{s^2R_2C_2C_1}{2} + \frac{sC_1}{2} + \frac{sC_2}{2} + \frac{1}{2R_2} - sC_1 - \frac{1}{2R_2} \right)$$

$$V_i = V_o \left( \frac{sR_2C_2}{2} + \frac{1}{2} + \frac{s^2R_2C_2C_1}{2} - \frac{sC_1}{2} + \frac{sC_2}{2} \right)$$

$$\frac{V_o(s)}{V_i(s)} = \frac{2}{sR_2C_2 + 1 + s^2R_1R_2C_1C_2 - sR_1C_1 + sR_1C_2}$$

$$c_1 = c_2$$

$$R_1 = R_2$$

$$\frac{V_o(jw)}{V_i(jw)} = \frac{2}{1 - w^2R_1R_2C_1C_2 + jwR_1C_2} = \frac{2}{1 - w^2 * 14.4 * 10^{-9} + jw0.12 * 10^{-3}}$$

$$|H(jw)| = \frac{2}{\sqrt{(1 - w^2 * 14.4 * 10^{-9})^2 + (w * 0.12 * 10^{-3})^2}}$$

$$|H(jw)| = \frac{|H(0)|}{\sqrt{2}} = \frac{2}{\sqrt{2}}$$

$$(1 - w^2 * 14.4 * 10^{-9})^2 + (w * 0.12 * 10^{-3})^2 = 0$$

$$w_c \cong 10600 \text{ rad/sec}$$

$$f_c \cong 1687 \text{ Hz}$$

Note! If we define  $w_c$  as;


$$|H(jw_c)| = \frac{|H(jw_c)|_{\max}}{\sqrt{2}} = \frac{2.3}{\sqrt{2}}$$

$$w_c \cong 9800 \text{ rad/sec}$$

$$f_c \cong 1560 \text{ Hz}$$

$$\angle H(jw) = -\tan^{-1} \left[ \frac{w * 0.12 * 10^{-3}}{1 - w^2 * 14.4 * 10^{-9}} \right]$$

## 2. Band-stop filter

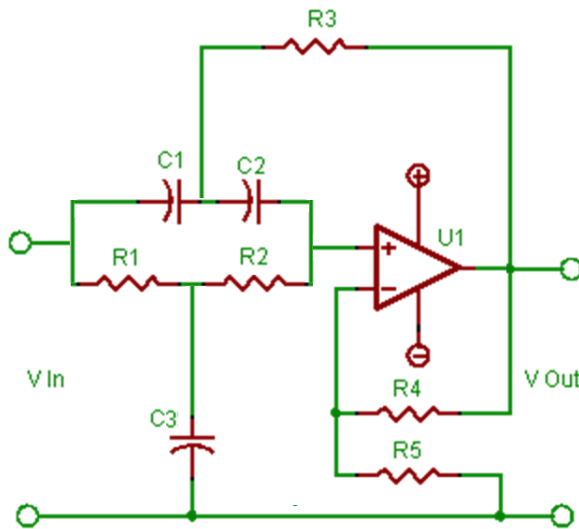

$$c_1 = c_2 = 0.5\mu\text{F}$$

$$c_3 = 1\mu\text{F}$$

$$R_1 = R_2 = 560\Omega$$

$$R_3 = 270\Omega$$

$$R_4 = 1\text{k}\Omega$$

$$R_5 = 2.2\text{k}\Omega$$

$$H(s) = K \frac{s^2 + \frac{1}{R_1 R_2 C_1 C_2}}{s^2 + s \left[ \frac{1-K}{R_3 C_1} + \frac{1}{R_2} \left( \frac{1}{C_1} + \frac{1}{C_2} \right) \right] + \frac{1}{R_1 R_2 C_1 C_2}}$$

$$K = 1 + \frac{R_4}{R_5} \cong 1.45$$

$$H(s) = 1.45 \frac{s^2 + 12.76 * 10^6}{s^2 + s * 3776 + 12.76 * 10^6}$$

$$H(j\omega) = 1.45 \frac{12.76 * 10^6 - \omega^2}{(12.76 * 10^6 - \omega^2) + j\omega * 3776}$$

$$|H(j\omega)| = 1.45 \frac{12.76 * 10^6 - \omega^2}{(12.76 * 10^6 - \omega^2)^2 + (\omega * 3776)^2}$$

$$\angle H(j\omega) = -\tan^{-1} \left[ \frac{3776\omega}{12.76 * 10^6 - \omega^2} \right]$$

$$|H(0)| = 1.45 \quad \implies \quad |H(j\omega)| = \frac{1.45}{\sqrt{2}} \cong 1$$


$$|H(j\omega)| = 1 \implies \omega_{c_1} \cong 2185\text{rad/sec}$$

$$\omega_{c_2} \cong 5840\text{rad/sec}$$

$$|H(j\omega_o)| = 0 \implies 12.76 * 10^6 - \omega_o^2 = 0 \implies \omega_o \cong 3571\text{rad/sec}$$

### 3. Band-pass filter

a.

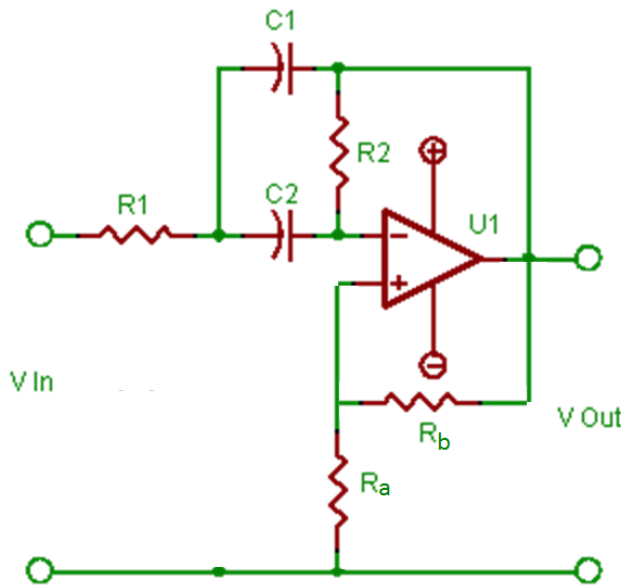

$$c_1 = c_2 = 4.7\text{nF}$$

$$R_1 = 1\text{k}\Omega$$

$$R_2 = 2.2\text{k}\Omega$$

$$R_a = R_b = 10\text{k}\Omega$$

$$V_+ = V_o \frac{R_a}{R_a + R_b} = \frac{V_o}{2} = V_- \quad \text{in linear mode}$$

1<sup>st</sup> node equation for  $V_- = \frac{V_o}{2}$  ;

$$\frac{V_o/2 - V_o}{R_2} + \frac{V_o/2 - V_x}{1/sC_2} = 0$$

$$V_x = V_o \left( \frac{1}{2} - \frac{1}{2sR_2C_2} \right) \quad (\text{eqn} - 1)$$

2<sup>nd</sup> node equation for  $V_x$  ;

$$\frac{V_x - V_o/2}{1/sC_1} + \frac{V_x - V_o}{1/sC_1} + \frac{V_x - V_i}{R_1} = 0$$

$$\frac{V_i}{R_1} = V_x \left( \frac{1}{R_1} + sC_1 + sC_2 \right) - V_o \left( sC_1 + \frac{sC_2}{2} \right)$$

$$\frac{V_i}{R_1} = V_o \left( \frac{1}{2} - \frac{1}{2sR_2C_2} \right) \left( \frac{1}{R_1} + sC_1 + sC_2 \right) - V_o \left( sC_1 + \frac{sC_2}{2} \right)$$

$$\frac{V_i}{R_1} = V_o \left( \frac{1}{2R_1} - \frac{1}{2sR_1R_2C_2} + \frac{sC_1}{2} - \frac{C_1}{2R_2C_2} + \frac{sC_2}{2} - \frac{1}{2R_2} - sC_1 - \frac{sC_2}{2} \right)$$

$$c_1 = c_2$$

$$V_i = V_o \left( \frac{sR_2C_2 - sR_1C_1 - sR_1C_2 - 1 - s^2R_2C_2^2R_1}{2sR_1R_2C_2} \right)$$

$$\frac{V_o(s)}{V_i(s)} = \frac{-2sR_2C_2w}{(s^2C_2^2R_1R_2)^2 + (sR_1C_1 + sR_1C_2 - sR_2C_2 + 1)^2}$$

$$\frac{V_o(jw)}{V_i(jw)} = \frac{-j2R_2C_2w}{(1 - w^2C_2^2R_1R_2)^2 + (jw2R_1C_1 - jwR_2C_2)^2}$$

$$|H(jw)| = \frac{2wR_2C_2}{\sqrt{(1 - w^2C_2^2R_1R_2)^2 + w^2(2R_1C_1 - R_2C_2)^2}}$$

$$\angle H(jw) = -90 - \tan^{-1} \left[ \frac{-w * 0.94 * 10^{-6}}{1 - w^2 * 4.86 * 10^{-11}} \right]$$

The standard form of the transfer function of a second order band-pass filter is as follows

$$\frac{Ks}{\left(\frac{s}{w_o}\right)^2 + 2\alpha\frac{s}{w_o} + 1}$$

$$w_o = \frac{1}{C_1\sqrt{R_1R_2}} \implies w_o \cong 143.4 \text{ krad/sec}$$

$$\text{at } w_o, |H(jw_o)| \cong 22$$


$$|H(jw_c)| = \frac{22}{\sqrt{2}} = 15.5$$

$$w_{c_1} \cong 134 \text{ krad/sec}$$

$$w_{c_2} \cong 154 \text{ krad/sec}$$

$$\Delta_w = w_{c_2} - w_{c_1} = 20 \text{ krad/sec}$$

b. in linear region  $V_+ = V_- = 0$

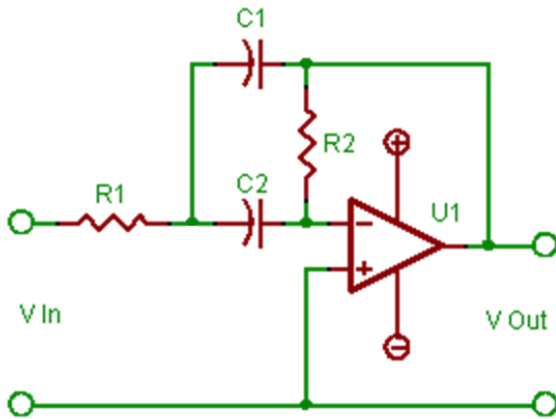

1<sup>st</sup> node equation for  $V_-$ ;

$$\frac{V_- - V_o}{R_2} + \frac{V_- - V_x}{1/sC_2} = 0$$

$$V_x = -\frac{V_o}{sR_2C_2} \quad (\text{eqn} - 1)$$

2<sup>nd</sup> node equation for  $V_x$ ;

$$\frac{V_x - V_+}{1/sC_1} + \frac{V_x - V_o}{1/sC_1} + \frac{V_x - V_i}{R_1} = 0$$

$$\frac{V_i}{R_1} = V_x \left( \frac{1}{R_1} + sC_1 + sC_2 \right) - V_o(sC_1)$$

$$\frac{V_i}{R_1} = -V_o \left( \frac{1}{R_2} + \frac{1}{sR_1R_2C_2} + \frac{C_1}{R_2C_2} + sC_1 \right)$$

$$V_i = -V_o \left( \frac{sR_1C_1 + 1 + sR_1C_2 + s^2R_2R_1C_2C_1}{sR_1R_2C_2} \right)$$

$$\frac{V_o(s)}{V_i(s)} = \frac{-sR_2C_2}{s^2C_1C_2R_1R_2 + sR_1C_1 + sR_1C_2 + 1}$$

$$H(j\omega) = \frac{-j\omega R_2C_2}{(1 - \omega^2 C_1C_2R_1R_2) + j\omega(R_1C_1 - R_2C_2)}$$

$$H(j\omega) = \frac{-j\omega * 10.34 * 10^{-6}}{(1 - \omega^2 * 4.86 * 10^{-11}) + j\omega * 9.4 * 10^{-6}}$$

$$|H(j\omega)| = \frac{-j\omega * 10.34 * 10^{-6}}{\sqrt{(1 - \omega^2 * 4.86 * 10^{-11})^2 + (\omega * 9.4 * 10^{-6})^2}}$$

$$\angle H(j\omega) = -90 - \tan^{-1} \left[ \frac{\omega * 9.4 * 10^{-6}}{1 - \omega^2 * 4.86 * 10^{-11}} \right]$$

The standard form of the transfer function of a second order filter:

$$\frac{Ks}{\left(\frac{s}{w_o}\right)^2 + 2\alpha\frac{s}{w_o} + 1}$$

$$w_o \cong 143.4 \text{ krad/sec}$$

$$\text{at } w_o, |H(jw_o)| \cong 1.1$$

$$|H(jw_c)| = \frac{1.1}{\sqrt{2}}$$

$$w_{c_1} \cong 76 \text{ krad/sec}$$

$$w_{c_2} \cong 270 \text{ krad/sec}$$

$$\Delta_w = w_{c_2} - w_{c_1} = 194 \text{ krad/sec}$$